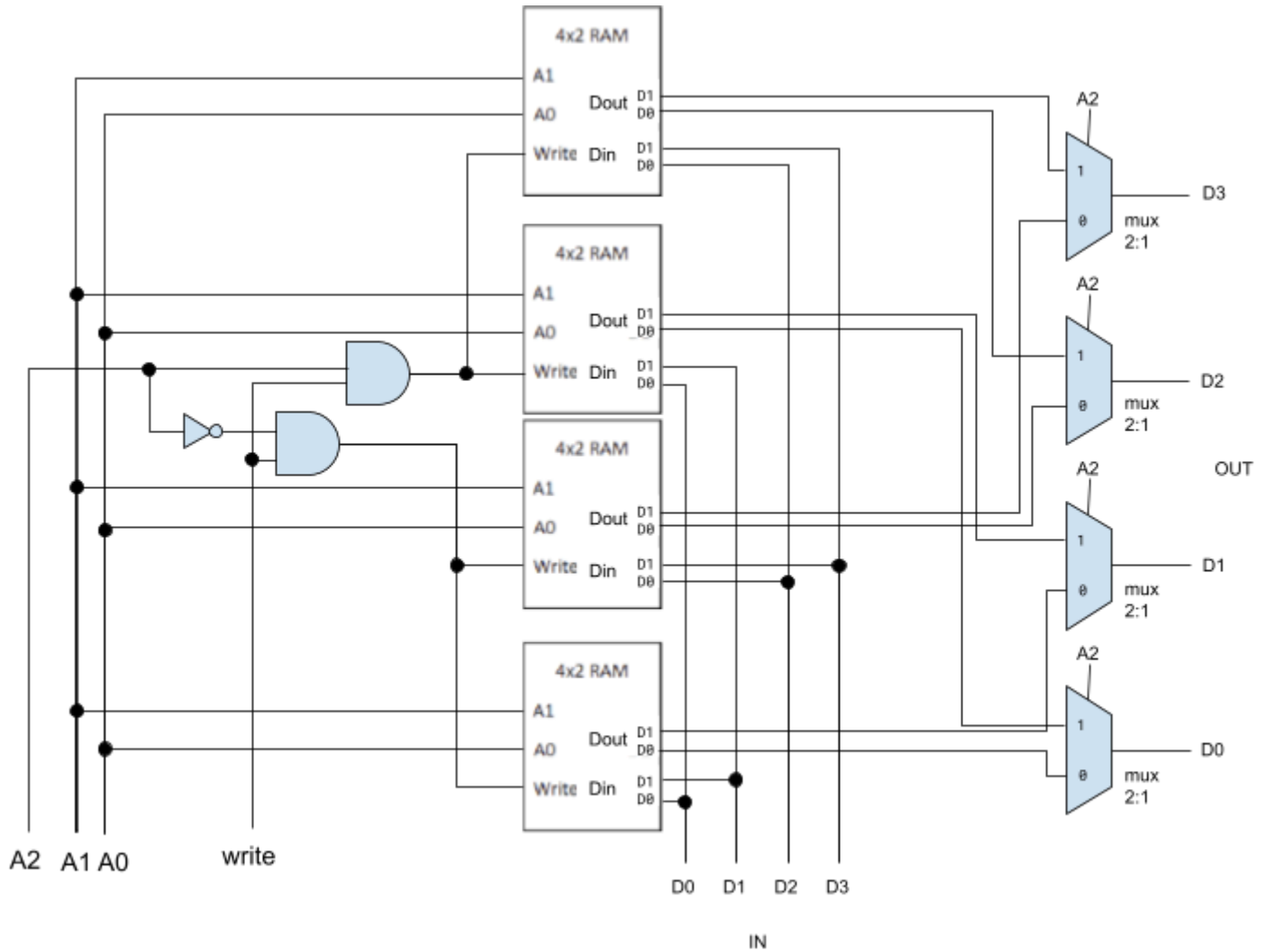


## EE/CSE 469 Computer Architecture I

## HW 1

**1. Design an 8x4 RAM using 4x2 RAMs (shown in the figure). You may use any number of RAM units as you need and any necessary combinational logic.**

**In the figure below, A1 and A0 specify bit 1 and 0 of the 2-bit address input of the 4x2 RAM, respectively. D1 and D0 represent bit 1 and 0 of its input/output data, respectively.**




2. Implement the following functions using a single 16x3 ROM. Use dot notation to indicate the ROM content.

a.  $X = AB + BC'D + A'B'$

b.  $Y = AB + BD$

c.  $Z = A + B + C + D$

 

**3. Consider memory storage of a 32-bit word stored at memory word 42 in a byte-addressable memory. Keep in mind the indexing method described in lecture.**

**a. What is the byte address of memory word 42?**

32 bits = 4 bytes,  $4 \times 42 = 168$  (Decimal), 0xA8 (Hex)

Memory word 42 has the address 0xA8

**b. What are the byte addresses that memory word 42 spans?**

0xA8 (Hex) + 4 bytes = 0xAC, Address of memory word 43

Memory word 42 spans from 0xA8 to 0xAB.

**c. Draw the number 0xFF223344 stored at word 42 in both big-endian and little-endian machines. Clearly label the byte address corresponding to each data byte value.**

Word Address	Data				Word Number
0xA8	44	33	22	FF	Word 42
	0xAB	0xAA	0xA9	0xA8	

big-endian

Word Address	Data				Word Number
0xA8	FF	22	33	44	Word 42
	0xAB	0xAA	0xA9	0xA8	

little-endian